

Attacking Glitch Detection Circuits

Amund Askeland

UNIVERSITY OF BERGEN



Attacking Glitch Detection Circuits

Who Watches the Watchers: Attacking Glitch Detection Circuits

Amund Askeland^{1,3}, Svetla Nikova^{1,2} and Ventzislav Nikov⁴

¹ University of Bergen, Bergen, Norway, firstname.lastname@uib.no

² COSIC, KU Leuven, Leuven, Belgium, firstname.lastname@esat.kuleuven.be


³ Nasjonal Sikkerhetsmyndighet, Oslo, Norway

⁴ NXP Semiconductors, Leuven, Belgium, vinci.nikov@gmail.com


- This talk is based on [ANN23]

Fault Injection Attacks

 - Provoke faulty computations in hardware
 - Some faults are exploitable
 - e.g faulty ciphertexts, incorrect branching
- Common methods are voltage and clock glitching
- Cause timing-violations in the target system




Timing in Hardware

 

Propagation Delay Due to Load Capacitance

$$t_{PLH} = \frac{C_L V_{DD}}{K_P (V_{DD} - V_{TP})^2}$$

Timing in Hardware

 


Timing Requirement for Synchronous Circuits

$$T_{clk} > T_{clk2Q} + T_{comb} + T_{setup}$$


Glitch Detection Circuits

 - Detectors as countermeasures
- A popular family of detector designs is based on "Parallel Delay Lines"




Glitch Detection Circuits

 
- Detectors as countermeasures
- A popular family of detector designs is based on "Parallel Delay Lines"



PDL-1

 

PDL-3

 


PDL-2

Attacking Glitch Detection Circuits

- The detectors work and can detect FIA
- Hard to prove a detector design
- Are there situations where these detectors can fail?

Clock Glitching

 - One or more glitches added to the clock signal
- We use T_G to refer to the time of extra *rising* edges





Experimental Setup

- Detectors and AES implemented on an FPGA
- Glitchy clock signal generated internally

| Fault Alarm | No | Yes |
|-------------|----------------|----------------|
| Low | Negative | False Negative |
| High | False Positive | Positive |

Attack 1

 
 
- Targets feedback inverter
- $T_G < T_{inv}$
- Applicable to PDL-1 and PDL-2



Attack 1 timing diagram


Attack 2

  - Between inverter and xor
- $T_{inv} + T_{setup} < T_G < T_{xor}$
- Applicable to PDL-1




Attack 2 timing diagram

Results Attack 1 & 2

 


PDL-1

 


PDL-2

Results Using External Glitch Generator

 

PDL-1. $V_{INT} = 1\text{ V}$

 



PDL-1. $V_{INT} = 0.93\text{ V}$

Double Glitch Attacks

- The single glitch attacks have strict requirements on T_G timing
- Using multiple glitches we have more options


Attack 3

  - Targets output xor
- $T_{G1} < T_D$ and $T_{G2} - T_{G1} < T_{xor}$
- Applicable to PDL-2 and PDL-3




Attack 3 timing diagram

Results Attack 3

 



PDL-2

 

PDL-3


Attack 4

  - Extension of attack 2
- $T_{inv} + T_{setup} < T_{G1} < T_{xor}$ and $T_{G1} + T_{xor} < T_{G2} < T_{xor} + T_D$
- Applicable to PDL-1



Attack 2 timing diagram

Results Attack 4

 

Conclusion

- Glitch detectors can fail
- There are countermeasures
- Room for improvement

References I



Amund Askeland, Svetla Nikova, and Ventzislav Nikov.
Who watches the watchers: Attacking glitch detection circuits.
Cryptology ePrint Archive, Paper 2023/1647, 2023.
<https://eprint.iacr.org/2023/1647>.

Questions?